

TP N°2: Voltímetro digital con salida VGA

Vázquez, Matías - 91523
mfvazquez@gmail.com

12 de diciembre de 2015

En el presente Trabajo Práctico se implementará en FPGA un sistema digital para un voltímetro digital con salida VGA.

1. Especificaciones

Se implementó en lenguaje descriptor de hardware VHDL un voltímetro digital con salida VGA. La tensión máxima que podrá mostrar el voltímetro es 3,3 V.

Se utilizó el kit de desarrollo “Spartan-3 Starter Board” de la empresa digilent. Utilizando una frecuencia de clock de 50 MHz.

2. Diseño

2.1. Diagrama en bloques general

A continuación, en la figura 1 se presenta el diagrama en bloques general del sistema. La tensión a ser mostrada por salida VGA es V_{in} que es conectada a la entrada no inversora del amplificador operacional. El amplificador operacional generará a través del Flip-Flop D un PWM de forma que el ciclo de trabajo generado sea equivalente a V_{in} . Por ejemplo: si $V_{in} = 3,3$ V el ciclo de trabajo será del 100 %; si $V_{in} = 1,65$ V el ciclo de trabajo será del 50 %;

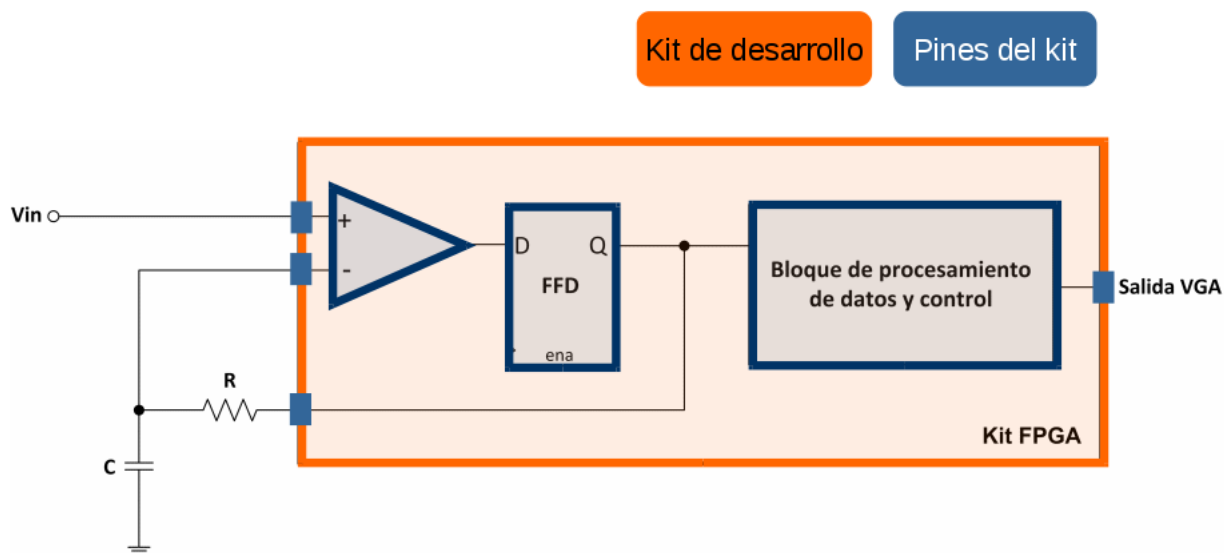


Figura 1: Diagrama en bloques general

3. Simulaciones

A continuación se muestran algunas simulaciones realizadas mediante pruebas.

3.1. Contador BCD

En esta simulación se comprobó que el contador BCD cuenta como un número decimal de 3 dígitos, cada dígito esta representado por 4 bits.

 


Figura 3: Simulación del contador BCD

3.2. Contador binario de N bits

Se verificó que los flags de salida de este bloque se ejecuten en el orden necesario. Como se verifica en la figura 4 primero se habilita el flag `out_1` que corresponde al registro, guardando así el valor de la salida del contador BCD en ese momento. Paso siguiente reinicia el contador BCD.

 


Figura 4: Simulación del contador binario de N bits

3.3. Multiplexor

Las entradas del multiplexor eran: "0000", "0000", "1000", "0100", "0010" y "0001". se fue incrementando en 1 los bits de selección desde 0 hasta 3. Se verificó que la salida del multiplexor correspondía a la siguiente secuencia: "0001", "0010", "0100" y "1000".

 


Figura 5: Simulación del multiplexor

3.4. Registro

Se verificó que la salida del registro es igual a la entrada cuando el flag `en_t` valía 1. Cuando valía 0 guardaba el último dato mostrado.

 


Figura 6: Simulación del registro

3.5. Sampler

Este bloque esta compuesto por el contador BCD, el contador binario de N bits y el registro. Se ingresó un PWM de 80 % y se verificó que la salida era 265, valor que corresponde a 2,65 V. Se puede comprobar que si un PWM del 100 % corresponde a 3,30 V entonces un PWM del 80 % corresponde a 2,64 V

 


Figura 7: Simulación del sampler

4. Resumen de síntesis

Utilización Lógica	Usados	Utilización
Slices	116	2 %
Flip-Flops	65	0 %
LUTs	213	2 %
GCLK	1	4 %

5. Código fuente VHDL

5.1. BCD.vhd

```
library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.numeric_std.all;

entity BCD is
    port(
        clk: in std_logic;
        rst: in std_logic;
        en: in std_logic;
        cuenta: out std_logic_vector(3 downto 0);
        flag: out std_logic
    );
end;

architecture BCD_arq of BCD is
    signal flag_aux: std_logic;
begin
    process(clk, rst, en)
        variable aux: unsigned(3 downto 0);
    begin
        if rst = '1' then
            aux := "0000";
            flag_aux <= '0';
        elsif rising_edge(clk) then
            if en = '1' then
                aux := aux + 1;
                if aux = "1001" then
                    flag_aux <= '1';
                elsif aux = "1010" then
                    aux := "0000";
                    flag_aux <= '0';
                end if;
            end if;
        end if;
        cuenta <= std_logic_vector(aux);
    end process;
    flag <= flag_aux and en;
end;
```

5.2. BCD3.vhd

```
library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.numeric_std.all;

entity BCD3 is
    port(
        clk: in std_logic;
        rst: in std_logic;
        en: in std_logic;
        cuenta: out std_logic_vector(11 downto 0)
    );
end;

architecture Beh of BCD3 is

    signal clk_aux: std_logic;
    signal rst_aux: std_logic;
    signal en_aux: std_logic_vector(3 downto 0);
    signal bcd_aux: std_logic_vector(11 downto 0);

    component BCD is
        port(
            clk: in std_logic;
            rst: in std_logic;
            en: in std_logic;
            cuenta: out std_logic_vector(3 downto 0);
            flag: out std_logic
        );
    end component;

begin

    en_aux(0) <= en;
    clk_aux <= clk;
    rst_aux <= rst;
    cuenta <= bcd_aux;

    bc3s_3:
    for i in 0 to 2 generate

        inst_BCD: BCD
            port map(
                clk => clk_aux,
                rst => rst_aux,
                en => en_aux(i),
                cuenta => bcd_aux(i*4+3 downto i*4),
                flag => en_aux(i+1)
            );

    end generate;

end;
```

5.3. BCD3_test.vhd

```
library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.numeric_std.all;

entity test_BCD3 is
end;

architecture Beh of test_BCD3 is
    signal clk_t: std_logic := '0';
    signal rst_t: std_logic := '1';
    signal en_t: std_logic := '1';
    signal bcd_t: std_logic_vector(11 downto 0);

    component BCD3 is
        port(
            clk: in std_logic;
            rst: in std_logic;
            en: in std_logic;
            cuenta: out std_logic_vector(11 downto 0)
        );
    end component;

begin

    inst_BCD3: BCD3
    port map(
        clk => clk_t,
        rst => rst_t,
        en => en_t,
        cuenta => bcd_t
    );

    clk_t <= not clk_t after 10 ns;
    rst_t <= '0' after 50 ns;

end;
```


5.4. Char_ROM.vhd

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity Char_ROM is
    generic(
        N: integer:= 6;
        M: integer:= 3;
        W: integer:= 8
    );
    port(
        char_address: in std_logic_vector(5 downto 0);
        font_row, font_col: in std_logic_vector(M-1 downto 0);
        rom_out: out std_logic
    );
end;

architecture p of Char_ROM is
    subtype tipoLinea is std_logic_vector(0 to W-1);

    type char is array(0 to W-1) of tipoLinea;
    constant Cero: char:= (
        "00011100",
        "00110110",
        "01100011",
        "01101011",
        "01100011",
        "00110110",
        "00011100",
        "00000000"
    );

    constant Uno: char:= (
        "00001100",
        "00111100",
        "00001100",
        "00001100",
        "00001100",
        "00001100",
        "00111111",
        "00000000"
    );

    constant Dos: char:= (
        "00111110",
        "01100011",
        "00000110",
        "00001100",
        "00011000",
        "00110000",
        "01111111",
        "00000000"
    );

    constant Tres: char:= (
        "01111111",
        "00000110",
        "00001100",
        "00000110",
```

```

                                );
    constant Cuatro: char:= (
                                "00000011",
                                "01100110",
                                "00111100",
                                "00000000"
                                );
                                "00000110",
                                "00001110",
                                "00010110",
                                "00100110",
                                "01111111",
                                "00000110",
                                "00000110",
                                "00000000"
                                );
    constant Cinco: char:= (
                                "01111111",
                                "01100000",
                                "01111110",
                                "00000011",
                                "00000011",
                                "01100110",
                                "00111100",
                                "00000000"
                                );
                                "00000110",
                                "00001100",
                                "00110000",
                                "01100000",
                                "01111110",
                                "01000011",
                                "00111100",
                                "00000000"
                                );
    constant Seis: char:= (
                                "01111111",
                                "00000110",
                                "00001100",
                                "00011000",
                                "01100000",
                                "01100000",
                                "01100000",
                                "00000000"
                                );
                                "00111110",
                                "01100011",
                                "01100011",
                                "01111111",
                                "01100011",
                                "01100011",
                                "00111110",
                                "00000000"
                                );
    constant Ocho: char:= (
                                "00111110",
                                "01100011",
                                "01100011",
                                "01111111",
                                "01100011",
                                "01100011",
                                "00111110",
                                "00000000"
                                );
                                "00111110",
                                "01100011",
                                "00111110",
                                "00000110",

```

```

                                "00000110" ,
                                "00011000" ,
                                "01100000" ,
                                "00000000"
                                );

constant Punto: char:= (
                                "00000000" ,
                                "00000000" ,
                                "00000000" ,
                                "00000000" ,
                                "00000000" ,
                                "00011000" ,
                                "00011000" ,
                                "00000000"
                                );

constant V: char:= (
                                "10000001" ,
                                "10000001" ,
                                "01000010" ,
                                "01000010" ,
                                "00100100" ,
                                "00100100" ,
                                "00011000" ,
                                "00000000"
                                );

constant Espacio: char:= (
                                "00000000" ,
                                "00000000" ,
                                "00000000" ,
                                "00000000" ,
                                "00000000" ,
                                "00000000" ,
                                "00000000" ,
                                "00000000"
                                );

type memo is array(0 to 255) of tipoLinea;
signal RAM: memo:= (
    0 => Cero(0), 1 => Cero(1), 2 => Cero(2), 3 => Cero(3),
    4 => Cero(4), 5 => Cero(5), 6 => Cero(6), 7 => Cero(7),

    8 => Uno(0), 9 => Uno(1), 10 => Uno(2), 11 => Uno(3),
    12 => Uno(4), 13 => Uno(5), 14 => Uno(6), 15 => Uno(7),

    16 => Dos(0), 17 => Dos(1), 18 => Dos(2), 19 => Dos(3),
    20 => Dos(4), 21 => Dos(5), 22 => Dos(6), 23 => Dos(7),

    24 => Tres(0), 25 => Tres(1), 26 => Tres(2), 27 => Tres(3),
    28 => Tres(4), 29 => Tres(5), 30 => Tres(6), 31 => Tres(7),

    32 => Cuatro(0), 33 => Cuatro(1), 34 => Cuatro(2), 35 => Cuatro(3),
    36 => Cuatro(4), 37 => Cuatro(5), 38 => Cuatro(6), 39 => Cuatro(7),

    40 => Cinco(0), 41 => Cinco(1), 42 => Cinco(2), 43 => Cinco(3),
    44 => Cinco(4), 45 => Cinco(5), 46 => Cinco(6), 47 => Cinco(7),

    48 => Seis(0), 49 => Seis(1), 50 => Seis(2), 51 => Seis(3),
    52 => Seis(4), 53 => Seis(5), 54 => Seis(6), 55 => Seis(7),

    56 => Siete(0), 57 => Siete(1), 58 => Siete(2), 59 => Siete(3),

```

```
        60 => Siete(4), 61 => Siete(5), 62 => Siete(6), 63 => Siete(7),

        64 => Ocho(0), 65 => Ocho(1), 66 => Ocho(2), 67 => Ocho(3),
        68 => Ocho(4), 69 => Ocho(5), 70 => Ocho(6), 71 => Ocho(7),

        72 => Nueve(0), 73 => Nueve(1), 74 => Nueve(2), 75 => Nueve(3),
        76 => Nueve(4), 77 => Nueve(5), 78 => Nueve(6), 79 => Nueve(7),

        80 => Punto(0), 81 => Punto(1), 82 => Punto(2), 83 => Punto(3),
        84 => Punto(4), 85 => Punto(5), 86 => Punto(6), 87 => Punto(7),

        88 => V(0), 89 => V(1), 90 => V(2), 91 => V(3), 92 => V(4),
        93 => V(5), 94 => V(6), 95 => V(7),

        96 => Espacio(0), 97 => Espacio(1), 98 => Espacio(2),
        99 => Espacio(3), 100 => Espacio(4), 101 => Espacio(5),
        102 => Espacio(6), 103 => Espacio(7),

        104 to 255 => "00000000"
    );

    signal char_addr_aux: std_logic_vector(8 downto 0);

begin

    char_addr_aux <= char_address & font_row;
    rom_out <= RAM(conv_integer(char_addr_aux))(conv_integer(font_col));

end;
```

5.5. CounterNb.vhd

```
library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.numeric_std.all;

entity CounterNb is
    port(
        clk: in std_logic;
        out1: out std_logic;
        out2: out std_logic := '0'
    );
end;

architecture Beh of CounterNb is
begin
    process(clk)
        variable rst: std_logic := '1';
        variable out_rst: unsigned(1 downto 0) := "10";
        variable cuenta: unsigned(8 downto 0) := (others => '0');

    begin
        if rising_edge(clk) then
            if out_rst = "01" then
                out1 <= '0';
                out_rst := "10";
            elsif out_rst = "10" then
                out2 <= '1';
                out_rst := "11";
            elsif out_rst = "11" then
                out2 <= '0';
                out_rst := "00";
            else
                cuenta := cuenta + 1;
                if rst = '1' then
                    cuenta := (others => '0');
                    rst := '0';
                    out_rst := "01";
                    out1 <= '1';
                elsif cuenta = "101001001" then
                    rst := '1';
                end if;
            end if;
        end if;
    end process;
end;
```

5.6. CounterNb_test.vhd

```
library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.numeric_std.all;

entity test_CounterNb is
end;

architecture beh of test_CounterNb is
    signal clk_t: std_logic := '0';
    signal out1_t: std_logic;
    signal out2_t: std_logic;

    component CounterNb is
        port(
            clk: in std_logic;
            out1: out std_logic := '0';
            out2: out std_logic := '0'
        );
    end component;

begin
    inst_CounterNb: CounterNb
        port map(
            clk => clk_t,
            out1 => out1_t,
            out2 => out2_t
        );
    clk_t <= not clk_t after 10 ns;
end;
```

5.7. FFD.vhd

```
library IEEE;
use IEEE.std_logic_1164.all;

entity FFD is
    port(
        clk: in std_logic;
        rst: in std_logic;
        ena: in std_logic;
        D: in std_logic;
        Q: out std_logic
    );
end FFD;

architecture beh of ffd is
begin
    process(clk, rst)
    begin
        if rst = '1' then
            Q <= '0';
        elsif rising_edge(clk) then
            if ena = '1' then
                Q <= D;
            end if;
        end if;
    end process;
end beh;
```

5.8. Logic.vhd

```
library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.numeric_std.all;

entity Logic is
    port(
        pixel_row, pixel_col: in std_logic_vector(9 downto 0);
        font_row, font_col: out std_logic_vector(2 downto 0);
        sel: out std_logic_vector(2 downto 0)
    );
end;

architecture Beh of Logic is
begin
    process(pixel_row, pixel_col)
        variable col, col_aux, fila, fila_aux, char_col, char_fila: unsigned(9 downto 0);
        variable pixel_col_aux, pixel_fila_aux: unsigned(2 downto 0);
    begin
        col := unsigned(pixel_col);
        fila := unsigned(pixel_row);
        col_aux := col mod 8;
        fila_aux := fila mod 8;
        char_col := col/8;
        char_fila := fila/8;

        pixel_col_aux := col_aux(2 downto 0);
        pixel_fila_aux := fila_aux(2 downto 0);
        font_row <= std_logic_vector(pixel_fila_aux);
        font_col <= std_logic_vector(pixel_col_aux);

        if char_fila = 30 then
            if char_col = 38 then
                sel <= "000";    -- (0) digito mas significativo
            elsif char_col = 39 then
                sel <= "011";    -- (3) punto
            elsif char_col = 40 then
                sel <= "001";    -- (1) primer decimal
            elsif char_col = 41 then
                sel <= "010";    -- (2) segundo decimal
            elsif char_col = 42 then
                sel <= "100";    -- (4) V
            else
                sel <= "101";    -- (5) espacio
            end if;
        else
            sel <= "101";        -- (5) espacio
        end if;
    end process;
end;
```


5.9. Mux.vhd

```
library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.numeric_std.all;

entity Mux is
    port(
        input: in std_logic_vector(23 downto 0);
        sel: in std_logic_vector(2 downto 0);
        output: out std_logic_vector(5 downto 0)
    );
end;

architecture Beh of Mux is

    signal sel_aux: std_logic_vector(2 downto 0);
    signal input_aux: std_logic_vector(23 downto 0);
    signal output_aux: std_logic_vector(5 downto 0);

    component Mux_gen is
        generic(
            inputs: natural := 16;
            data_bus: natural := 4;
            sel_length: natural := 2
        );
        port(
            input: in std_logic_vector(inputs-1 downto 0);
            sel: in std_logic_vector(sel_length-1 downto 0);
            output: out std_logic_vector(data_bus-1 downto 0)
        );
    end component;

begin

    inst_Mux_gen: Mux_gen
        generic map(
            inputs => 24,
            data_bus => 4,
            sel_length => 3
        )
        port map(
            input => input_aux,
            sel => sel_aux,
            output => output_aux(3 downto 0)
        );

    output_aux(5 downto 4) <= "00";
    output <= output_aux;
    input_aux <= input;
    sel_aux <= sel;

end;
```

5.10. Mux_gen.vhd

```
library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.numeric_std.all;

entity Mux_gen is
    generic(
        inputs: natural := 16;
        data_bus: natural := 4;
        sel_length: natural := 2
    );
    port(
        input: in std_logic_vector(inputs-1 downto 0);
        sel: in std_logic_vector(sel_length-1 downto 0);
        output: out std_logic_vector(data_bus-1 downto 0)
    );
end;

architecture Beh of Mux_gen is
begin
    process(sel, input)
        variable sel_aux: unsigned(sel_length-1 downto 0);
        variable fin, inicio: natural;
        begin
            sel_aux := unsigned(sel);
            inicio := to_integer(sel_aux);
            inicio := inicio * data_bus;
            fin := inicio + data_bus - 1;

            output <= input(fin downto inicio);
        end process;
end;
```

5.11. Mux_test.vhd

```
library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.numeric_std.all;

entity test_Mux is
end;

architecture Beh of test_Mux is
    signal sel_t: std_logic_vector(2 downto 0) := "000";
    signal input_t: std_logic_vector(23 downto 0) := "000000001000010000100001";
    signal output_t: std_logic_vector(5 downto 0);

    component Mux is
        port(
            input: in std_logic_vector(23 downto 0);
            sel: in std_logic_vector(2 downto 0);
            output: out std_logic_vector(5 downto 0)
        );
    end component;

begin

    inst_Mux: Mux
        port map(
            input => input_t,
            sel => sel_t,
            output => output_t
        );
    sel_t(0) <= not sel_t(0) after 10 ns;
    sel_t(1) <= not sel_t(1) after 20 ns;

end;
```

5.12. Process_and_controll.vhd

```
library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.numeric_std.all;

entity Process_and_controll is
    port(
        en: in std_logic;
        clk: in std_logic;
        hs: out std_logic;
        vs: out std_logic;
        red_o: out std_logic_vector(2 downto 0);
        grn_o: out std_logic_vector(2 downto 0);
        blu_o: out std_logic_vector(1 downto 0)
    );
end;

architecture Beh of Process_and_controll is

    signal en_aux: std_logic;
    signal clk_aux: std_logic;
    signal output_aux: std_logic_vector(11 downto 0);
    signal input_aux: std_logic_vector(23 downto 0);
    signal hs_aux: std_logic;
    signal vs_aux: std_logic;
    signal red_o_aux: std_logic_vector(2 downto 0);
    signal grn_o_aux: std_logic_vector(2 downto 0);
    signal blu_o_aux: std_logic_vector(1 downto 0);

    component Sampler is
        port(
            en: in std_logic;
            clk: in std_logic;
            output: out std_logic_vector(11 downto 0)
        );
    end component;

    component VGA_volt is
        port(
            mclk: in std_logic;
            input: in std_logic_vector(23 downto 0);
            hs: out std_logic;
            vs: out std_logic;
            red_o: out std_logic_vector(2 downto 0);
            grn_o: out std_logic_vector(2 downto 0);
            blu_o: out std_logic_vector(1 downto 0)
        );
    end component;

begin

    en_aux <= en;
    clk_aux <= clk;
    hs <= hs_aux;
    vs <= vs_aux;
    red_o <= red_o_aux;
    grn_o <= grn_o_aux;
    blu_o <= blu_o_aux;
```

```
input_aux(11 downto 8) <= output_aux(3 downto 0);
input_aux(7 downto 4) <= output_aux(7 downto 4);
input_aux(3 downto 0) <= output_aux(11 downto 8);

input_aux(15 downto 12) <= "1010"; — direccion en memoria del caracter: '.'
input_aux(19 downto 16) <= "1011"; — direccion en memoria del caracter: 'V'
input_aux(23 downto 20) <= "1100"; — direccion en memoria del caracter: ' '

inst_Sampler: Sampler
  port map(
    en => en_aux,
    clk => clk_aux,
    output => output_aux
  );

inst_VGA_volt: VGA_volt
  port map(
    mclk => clk_aux,
    input => input_aux,
    hs => hs_aux,
    vs => vs_aux,
    red_o => red_o_aux,
    grn_o => grn_o_aux,
    blu_o => blu_o_aux
  );

end;
```

5.13. Reg.vhd

```
library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.numeric_std.all;

entity Reg is
    port(
        clk: in std_logic;
        en: in std_logic;
        input: in std_logic_vector(11 downto 0);
        output: out std_logic_vector(11 downto 0)
    );
end;

architecture Beh of Reg is
begin
    process(clk, en)
    begin
        if rising_edge(clk) and en = '1' then
            output <= input;
        end if;
    end process;
end;
```

5.14. Reg_test.vhd

```
library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.numeric_std.all;

entity test_Reg is
end;

architecture Beh of test_Reg is
    signal clk_t: std_logic := '0';
    signal rst_t: std_logic := '1';
    signal en_t: std_logic := '1';
    signal en_bcd_t: std_logic := '1';
    signal input_t: std_logic_vector(11 downto 0);
    signal output_t: std_logic_vector(11 downto 0);

    component Reg is
        port(
            clk: in std_logic;
            en: in std_logic;
            input: in std_logic_vector(11 downto 0);
            output: out std_logic_vector(11 downto 0)
        );
    end component;

    component BCD3 is
        port(
            clk: in std_logic;
            rst: in std_logic;
            en: in std_logic;
            cuenta: out std_logic_vector(11 downto 0)
        );
    end component;

begin

    inst_Reg: Reg
    port map(
        clk => clk_t,
        en => en_t,
        input => input_t,
        output => output_t
    );

    inst_BCD3: BCD3
    port map(
        clk => clk_t,
        rst => rst_t,
        en => en_bcd_t,
        cuenta => input_t
    );

    clk_t <= not clk_t after 10 ns;
    rst_t <= '0' after 50 ns;
    en_t <= not en_t after 100 ns;
```

end;

5.15. Sampler.vhd

```
library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.numeric_std.all;

entity Sampler is
    port(
        en: in std_logic;
        clk: in std_logic;
        out_aux: out std_logic_vector(11 downto 0);
        output: out std_logic_vector(11 downto 0)
    );
end;

architecture Beh of Sampler is
    signal out1_aux: std_logic;
    signal out2_aux: std_logic;
    signal clk_aux: std_logic;
    signal en_aux: std_logic;
    signal input_aux: std_logic_vector(11 downto 0);
    signal output_aux: std_logic_vector(11 downto 0);

    component BCD3 is
        port(
            clk: in std_logic;
            rst: in std_logic;
            en: in std_logic;
            cuenta: out std_logic_vector(11 downto 0)
        );
    end component;

    component Reg is
        port(
            clk: in std_logic;
            en: in std_logic;
            input: in std_logic_vector(11 downto 0);
            output: out std_logic_vector(11 downto 0)
        );
    end component;

    component CounterNb is
        port(
            clk: in std_logic;
            out1: out std_logic;
            out2: out std_logic
        );
    end component;

begin
    clk_aux <= clk;
    en_aux <= en;
    output <= output_aux;
    out_aux <= input_aux;

    inst_CounterNb: CounterNb
        port map(
            clk => clk_aux,
            out1 => out1_aux,
            out2 => out2_aux
```

```
    );  
  
    inst_BCD3: BCD3  
    port map(  
        clk => clk_aux ,  
        rst => out2_aux ,  
        en => en_aux ,  
        cuenta => input_aux  
    );  
  
    inst_Reg: Reg  
    port map(  
        clk => clk_aux ,  
        en => out1_aux ,  
        input => input_aux ,  
        output => output_aux  
    );  
  
end;
```

5.16. Sampler_test.vhd

```
library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.numeric_std.all;

entity test_Sampler is
end;

architecture beh of test_Sampler is
    signal clk_t: std_logic := '0';
    signal en_t: std_logic;
    signal out_t: std_logic_vector(11 downto 0);
    signal out_aux_t: std_logic_vector(11 downto 0);

    component Sampler is
        port(
            en: in std_logic;
            clk: in std_logic;
            out_aux: out std_logic_vector(11 downto 0);
            output: out std_logic_vector(11 downto 0)
        );
    end component;

    component GenEna
        generic(
            N: natural := 2;
            M: natural := 1
        );
        port(
            clk: in std_logic;
            en: out std_logic
        );
    end component;

begin
    inst_Sampler: Sampler
        port map(
            en => en_t,
            clk => clk_t,
            out_aux => out_aux_t,
            output => out_t
        );

    inst_genEna: GenEna
        generic map(
            N => 2,
            M => 1
        )
        port map(
            clk => clk_t,
            en => en_t
        );

    clk_t <= not clk_t after 10 ns;
end;
```

5.17. VGActrl.vhd

```
— Modulo: Controlador VGA
— Descripcion:
— Autor: Sistemas Digitales (66.17)
— Universidad de Buenos Aires – Facultad de Ingenieria
— www.campus.fi.uba.ar
— Fecha: 16/04/13
```

```
library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.numeric_std.all;
```

```
entity vga_ctrl is
    port (
        mclk: in std_logic;
        red_i: in std_logic;
        grn_i: in std_logic;
        blu_i: in std_logic;
        hs: out std_logic;
        vs: out std_logic;
        red_o: out std_logic_vector(2 downto 0);
        grn_o: out std_logic_vector(2 downto 0);
        blu_o: out std_logic_vector(1 downto 0);
        pixel_row: out std_logic_vector(9 downto 0);
        pixel_col: out std_logic_vector(9 downto 0)
    );
```

```
end vga_ctrl;
```

```
architecture vga_ctrl_arq of vga_ctrl is
```

```
— Numero de pixeles en una linea horizontal (800)
constant hpixels: unsigned(9 downto 0) := "1100100000";
— Numero de lineas horizontales en el display (521)
constant vlines: unsigned(9 downto 0) := "1000001001";

constant hbp: unsigned(9 downto 0) := "0010010000";
— Back porch horizontal (144)
constant hfp: unsigned(9 downto 0) := "1100010000";
— Front porch horizontal (784)
constant vbp: unsigned(9 downto 0) := "0000011111";
— Back porch vertical (31)
constant vfp: unsigned(9 downto 0) := "0111111111";
— Front porch vertical (511)

— Contadores (horizontal y vertical)
signal hc, vc: unsigned(9 downto 0);
— Flag para obtener una habilitacion cada dos ciclos de clock
signal clkdiv_flag: std_logic;
— Senal para habilitar la visualizacion de datos
signal vidon: std_logic;
— Senal para habilitar el contador vertical
signal vsenable: std_logic;
```

```
begin
```

```

— Division de la frecuencia del reloj
process(mclk)
begin
    if rising_edge(mclk) then
        clkdiv_flag <= not clkdiv_flag;
    end if;
end process;

— Contador horizontal
process(mclk)
begin
    if rising_edge(mclk) then
        if clkdiv_flag = '1' then
            if hc = hpixels then
                hc <= (others => '0');
                vsenable <= '1';
                — Habilitacion del cont vert
            else
                hc <= hc + 1;
                — Incremento del cont horiz
                vsenable <= '0';
                — El cont vert se mantiene deshabilitado
            end if;
        end if;
    end if;
end process;

— Contador vertical
process(mclk)
begin
    if rising_edge(mclk) then
        if clkdiv_flag = '1' then
            if vsenable = '1' then
                if vc = vlimes then
                    vc <= (others => '0');
                else
                    vc <= vc + 1;
                end if;
            end if;
        end if;
    end if;
end process;

hs <= '1' when (hc < "0001100001") else '0';
vs <= '1' when (vc < "0000000011") else '0';

pixel_col <= std_logic_vector(hc - 144) when (vidon = '1')
            else std_logic_vector(hc);
pixel_row <= std_logic_vector(vc - 31) when (vidon = '1')
            else std_logic_vector(vc);

vidon <= '1' when (((hc < hfp) and (hc > hbp)) and ((vc < vfp) and (vc > vbp)))
            else '0';

red_o <= (others => '1') when (red_i = '1' and vidon = '1')
        else (others => '0');
grn_o <= (others => '1') when (grn_i = '1' and vidon = '1')
        else (others => '0');
blu_o <= (others => '1') when (blu_i = '1' and vidon = '1')

```

```
        else (others => '0');  
  
end vga_ctrl_arq;
```

5.18. VGA_volt.vhd

```
library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.numeric_std.all;

entity VGA_volt is
    port(
        mclk: in std_logic;
        input: in std_logic_vector(23 downto 0);
        hs: out std_logic;
        vs: out std_logic;
        red_o: out std_logic_vector(2 downto 0);
        grn_o: out std_logic_vector(2 downto 0);
        blu_o: out std_logic_vector(1 downto 0)
    );
end;

architecture Beh of VGA_volt is

    signal mclk_aux: std_logic;
    signal hs_aux: std_logic;
    signal vs_aux: std_logic;
    signal red_o_aux: std_logic_vector(2 downto 0);
    signal grn_o_aux: std_logic_vector(2 downto 0);
    signal blu_o_aux: std_logic_vector(1 downto 0);
    signal pixel_row_aux: std_logic_vector(9 downto 0);
    signal pixel_col_aux: std_logic_vector(9 downto 0);

    signal char_address_aux: std_logic_vector(5 downto 0);
    signal font_row_aux, font_col_aux: std_logic_vector(2 downto 0);
    signal rom_out_aux: std_logic;

    signal input_aux: std_logic_vector(23 downto 0);
    signal sel_aux: std_logic_vector(2 downto 0);

    component vga_ctrl is
        port (
            mclk: in std_logic;
            red_i: in std_logic;
            grn_i: in std_logic;
            blu_i: in std_logic;
            hs: out std_logic;
            vs: out std_logic;
            red_o: out std_logic_vector(2 downto 0);
            grn_o: out std_logic_vector(2 downto 0);
            blu_o: out std_logic_vector(1 downto 0);
            pixel_row: out std_logic_vector(9 downto 0);
            pixel_col: out std_logic_vector(9 downto 0)
        );
    end component;

    component Mux is
        port(
            input: in std_logic_vector(23 downto 0);
            sel: in std_logic_vector(2 downto 0);
            output: out std_logic_vector(5 downto 0)
        );
    end component;
```

```
    component Logic is
        port(
            pixel_row, pixel_col: in std_logic_vector(9 downto 0);
            font_row, font_col: out std_logic_vector(2 downto 0);
            sel: out std_logic_vector(2 downto 0)
        );
    end component;

    component Char_ROM is
        generic(
            N: integer:= 6;
            M: integer:= 3;
            W: integer:= 8
        );
        port(
            char_address: in std_logic_vector(5 downto 0);
            font_row, font_col: in std_logic_vector(M-1 downto 0);
            rom_out: out std_logic
        );
    end component;

begin

    input_aux <= input;
    hs <= hs_aux;
    vs <= vs_aux;
    red_o <= red_o_aux;
    grn_o <= grn_o_aux;
    blu_o <= blu_o_aux;
    mclk_aux <= mclk;

    inst_vga_ctrl: vga_ctrl
        port map (
            mclk => mclk_aux,
            red_i => rom_out_aux,
            grn_i => rom_out_aux,
            blu_i => '1',
            hs => hs_aux,
            vs => vs_aux,
            red_o => red_o_aux,
            grn_o => grn_o_aux,
            blu_o => blu_o_aux,
            pixel_row => pixel_row_aux,
            pixel_col => pixel_col_aux
        );

    inst_Mux: Mux
        port map(
            input => input_aux,
            sel => sel_aux,
            output => char_address_aux
        );

    inst_Logic: Logic
        port map(
            pixel_row => pixel_row_aux,
            pixel_col => pixel_col_aux,
            font_row => font_row_aux,
```



```
        font_col => font_col_aux ,  
        sel => sel_aux  
    );  
  
inst_Char_ROM: Char_ROM  
port map(  
    char_address => char_address_aux ,  
    font_row => font_row_aux ,  
    font_col => font_col_aux ,  
    rom_out => rom_out_aux  
);  
  
end;
```

5.19. Volt.vhd

```
library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.numeric_std.all;

entity VOLT is
    port(
        clk50: in std_logic;
        data_volt_in_p, data_volt_in_n: in std_logic;
        data_volt_out: out std_logic;
        hs: out std_logic;
        vs: out std_logic;
        red_o: out std_logic_vector(2 downto 0);
        grn_o: out std_logic_vector(2 downto 0);
        blu_o: out std_logic_vector(1 downto 0)
    );

    attribute loc: string;
    attribute slew: string;
    attribute drive: string;
    attribute iostandard: string;
    attribute loc of clk50: signal is "B8";

    attribute iostandard of data_volt_in_p: signal is "LVDS_25";
    attribute loc of data_volt_in_p: signal is "N18";
    attribute iostandard of data_volt_in_n: signal is "LVDS_25";
    attribute loc of data_volt_in_n: signal is "M18";

    attribute loc of data_volt_out: signal is "P18";
    attribute slew of data_volt_out: signal is "FAST";
    attribute drive of data_volt_out: signal is "8";
    attribute iostandard of data_volt_out: signal is "LVCMOS25";

    attribute loc of hs: signal is "T4";
    attribute loc of vs: signal is "U3";
    attribute loc of red_o: signal is "R8_T8_R9";
    attribute loc of grn_o: signal is "P6_P8_N8";
    attribute loc of blu_o: signal is "U4_U5";

end VOLT;

architecture beh of VOLT is

    component IBUFDS
        port(
            I : in std_logic;
            IB : in std_logic;
            O : out std_logic
        );
    end component;

    component FFD is
        port(
            clk: in std_logic;
            rst: in std_logic;
            ena: in std_logic;
            D: in std_logic;
            Q: out std_logic
```

```
    );  
end component;  
  
component Process_and_controll is  
    port (  
        en: in std_logic;  
        clk: in std_logic;  
        hs: out std_logic;  
        vs: out std_logic;  
        red_o: out std_logic_vector(2 downto 0);  
        grn_o: out std_logic_vector(2 downto 0);  
        blu_o: out std_logic_vector(1 downto 0)  
    );  
end component;  
  
signal Diff_Input: std_logic;  
signal process_in: std_logic;  
  
begin  
    ibuf0: IBUFDS port map(  
        I => data_volt_in_p ,  
        IB => data_volt_in_n ,  
        O => Diff_Input  
    );  
  
    inst_flop: FFD  
        port map(  
            clk => clk50 ,  
            rst => '0',  
            ena => '1',  
            D => Diff_Input ,  
            Q => process_in  
        );  
  
    inst_proces: Process_and_controll  
        port map(  
            process_in ,  
            clk50 ,  
            hs ,  
            vs ,  
            red_o ,  
            grn_o ,  
            blu_o  
        );  
  
    data_volt_out <= process_in;  
  
end;
```